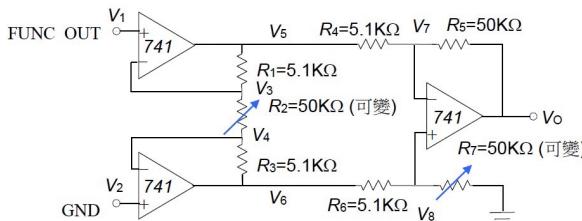


Lab 4 Differential Amplifier

1. Differential amplifier circuit diagram

Spec: gain should be at least $40 \text{ dB} = 100 \sqrt{\text{v}}$




To simplify the problem, make $R_7 = R_5 \Rightarrow$


Total gain of instrumentation amplifier is $\left(\frac{R_1+R_2+R_3}{R_2}\right) \cdot \left(\frac{R_5}{R_4}\right)$

WLOG set $R_2 = 51 \text{ k}\Omega$, $R_5 = R_7 = 510 \text{ k}\Omega$ to meet the specification.

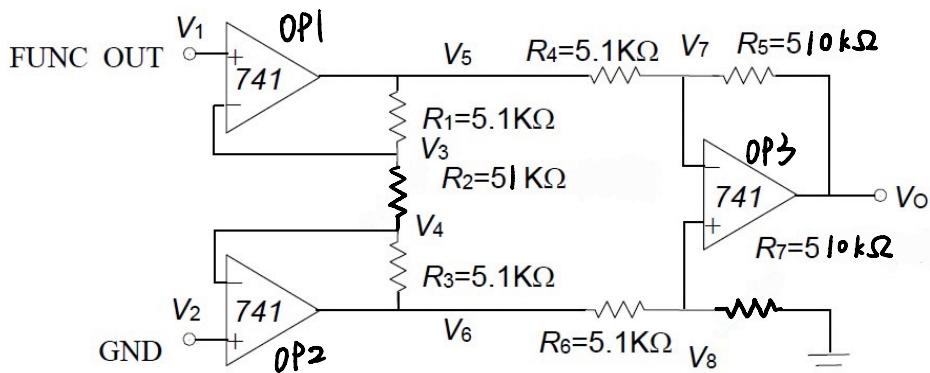
$$\begin{aligned} \text{Thus, the total gain} &= \left(\frac{5.1k + 51k + 5.1k}{51k}\right) \cdot \left(\frac{510k}{5.1k}\right) \\ &= 1.2 \cdot 100 = 120 (\sqrt{\text{v}}) \end{aligned}$$



Physical circuit:

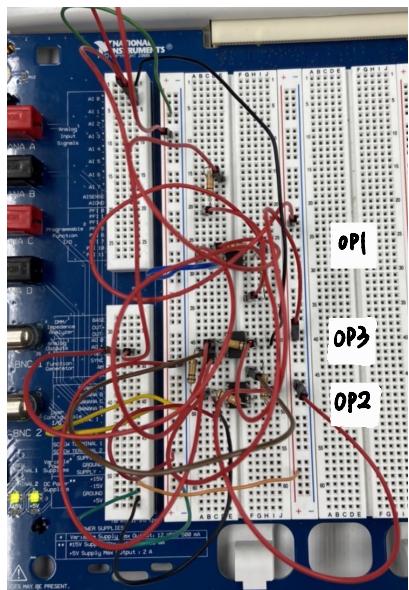

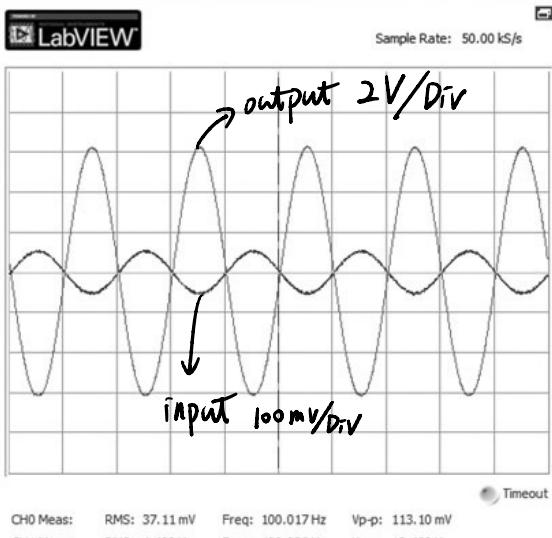
$$\text{Input } 100 \text{ Hz, } 0.1 \text{ Vpp, } A_{100\text{Hz}} = \frac{12.468}{0.113} = 110 \frac{\text{V}}{\text{V}}$$



input 10000 Hz, 0.1 Vpp.

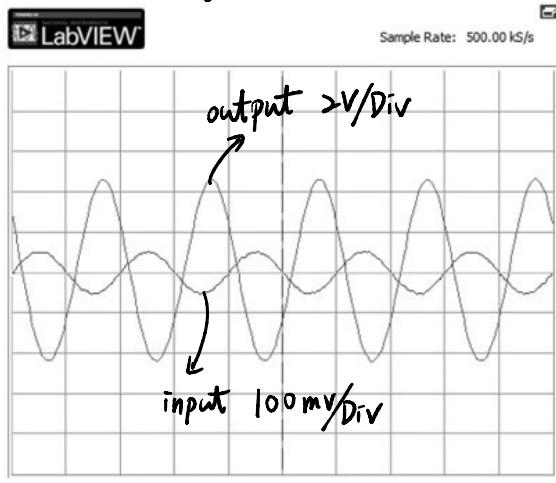
$$A_{10\text{kHz}} = \frac{9.059}{0.106} = 85.46 \frac{\text{V}}{\text{V}}$$



| | | | |
|-----------|---------------|------------------|-----------------|
| CH0 Meas: | RMS: 36.27 mV | Freq: 9.999 kHz | Vp-p: 106.73 mV |
| CH1 Meas: | RMS: 3.179 V | Freq: 10.002 kHz | Vp-p: 9.059 V |

input 15000 Hz, 0.1 Vpp


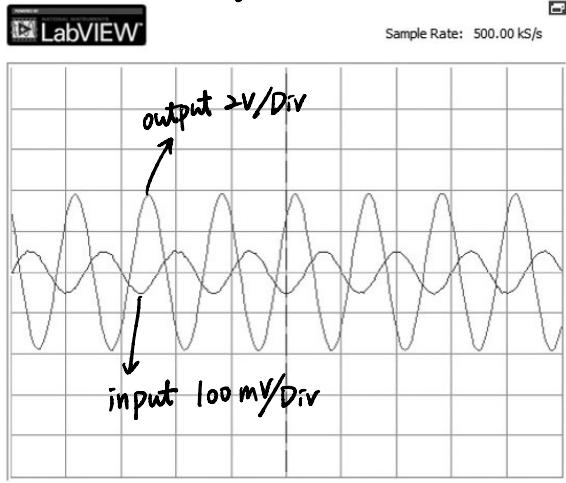
$$A_{15\text{kHz}} = \frac{7.707}{0.106} = 72.69 \frac{\text{V}}{\text{V}}$$



| | | | |
|-----------|---------------|------------------|-----------------|
| CH0 Meas: | RMS: 36.23 mV | Freq: 15.000 kHz | Vp-p: 106.24 mV |
| CH1 Meas: | RMS: 2.705 V | Freq: 14.999 kHz | Vp-p: 7.707 V |

Physical circuit bode plot

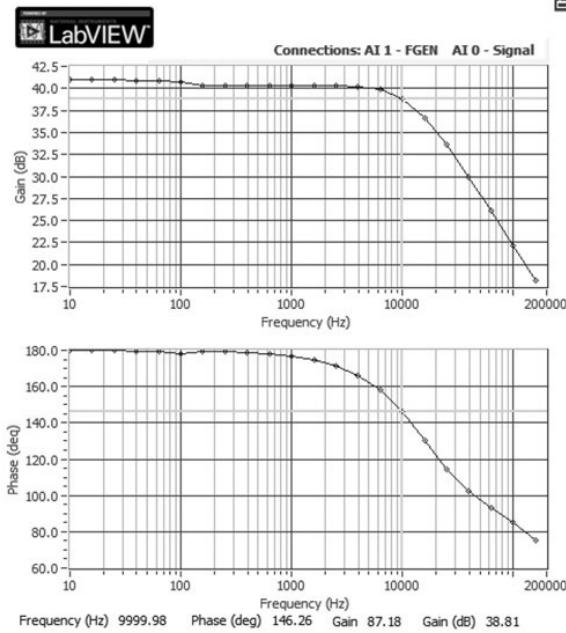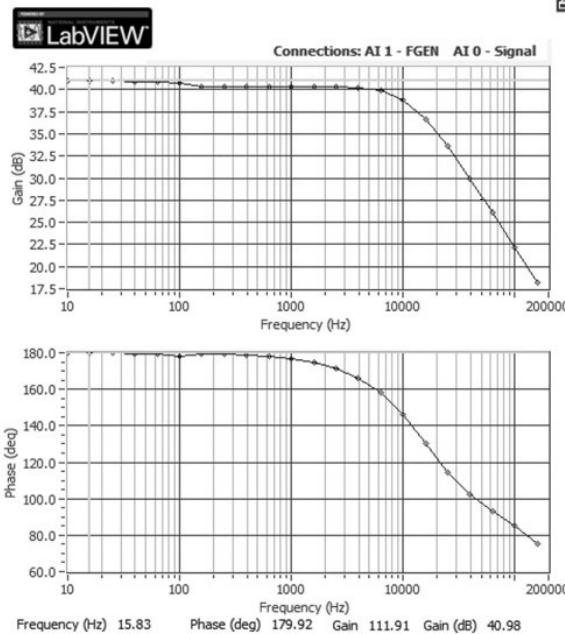Max gain $\approx 41 \text{ dB} = 10^{\frac{41}{20}} \approx 112.2 (\frac{V}{V})$ $\rightarrow -3 \text{ dB}$ point at 38 dB with $f_0 \approx 10 \text{ kHz}$




* Compare to three frequencies result

| f | Gain ($\frac{V}{V}$) | Bode Plot Gain |
|-------|------------------------|---|
| 100Hz | 110 | $41 \text{ dB} \approx 112 (\frac{V}{V})$ |
| 10kHz | 85 | $38 \text{ dB} \approx 80 (\frac{V}{V})$ |
| 15kHz | 72 | $36 \text{ dB} \approx 63 (\frac{V}{V})$ |

It's obviously that 3 frequency results match bode plot.


Differential Mode Multisim Simulation

Schematic :

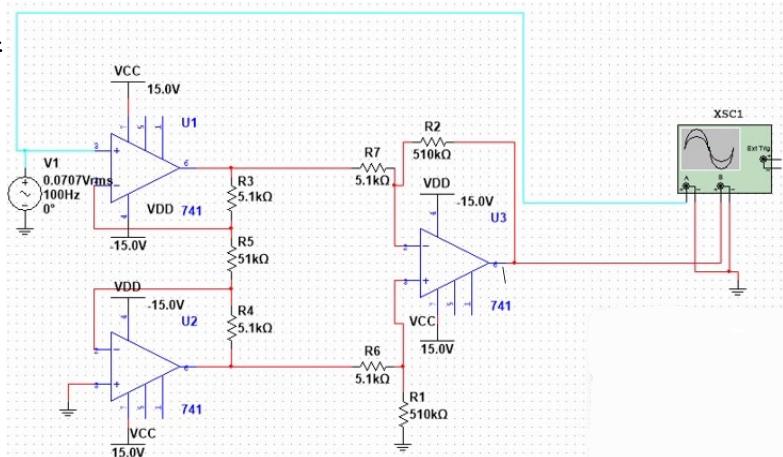


Input
100 Hz
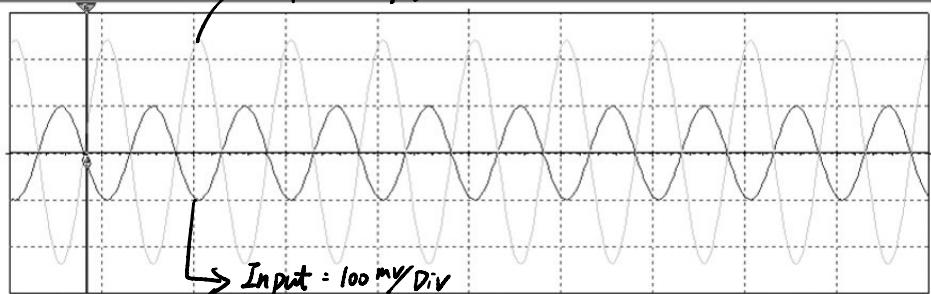
$$A_{100\text{Hz}} \approx 120 \frac{\text{V}}{\text{V}}$$




Input
10 kHz
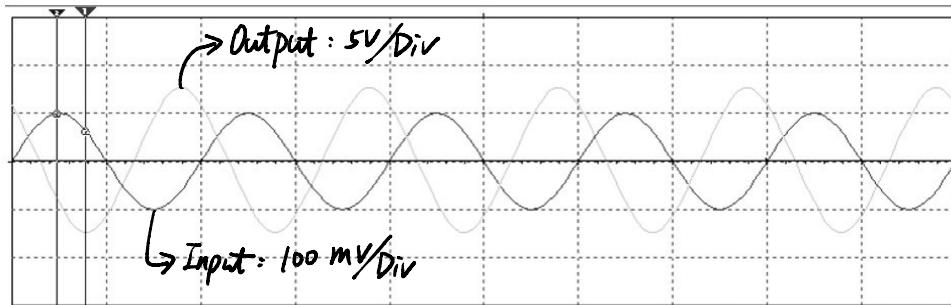
$$A_{10\text{kHz}} \approx 80 \frac{\text{V}}{\text{V}}$$




Input
15 kHz
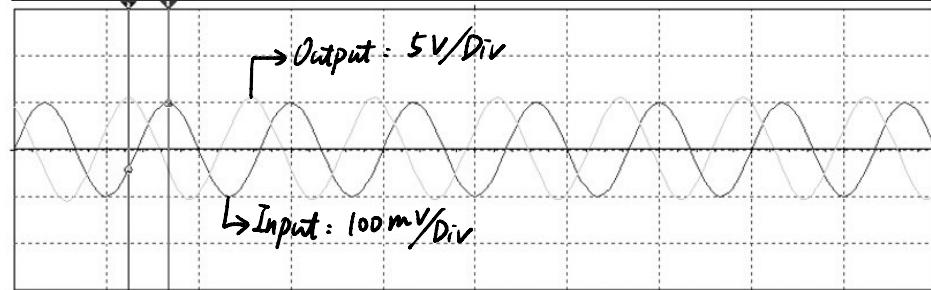
$$A_{15\text{kHz}} \approx 60 \frac{\text{V}}{\text{V}}$$




Bode Plot - Magnitude Response

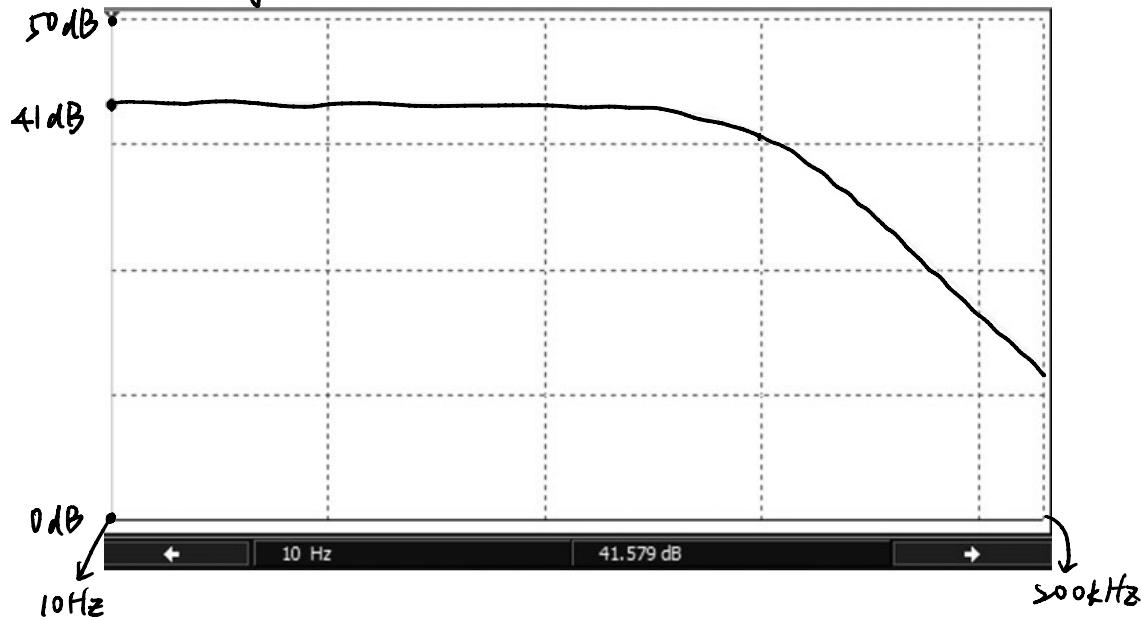Peak gain at $f = 10\text{ Hz}$, $A = 41.579\text{ dB} \approx 119.9\%$




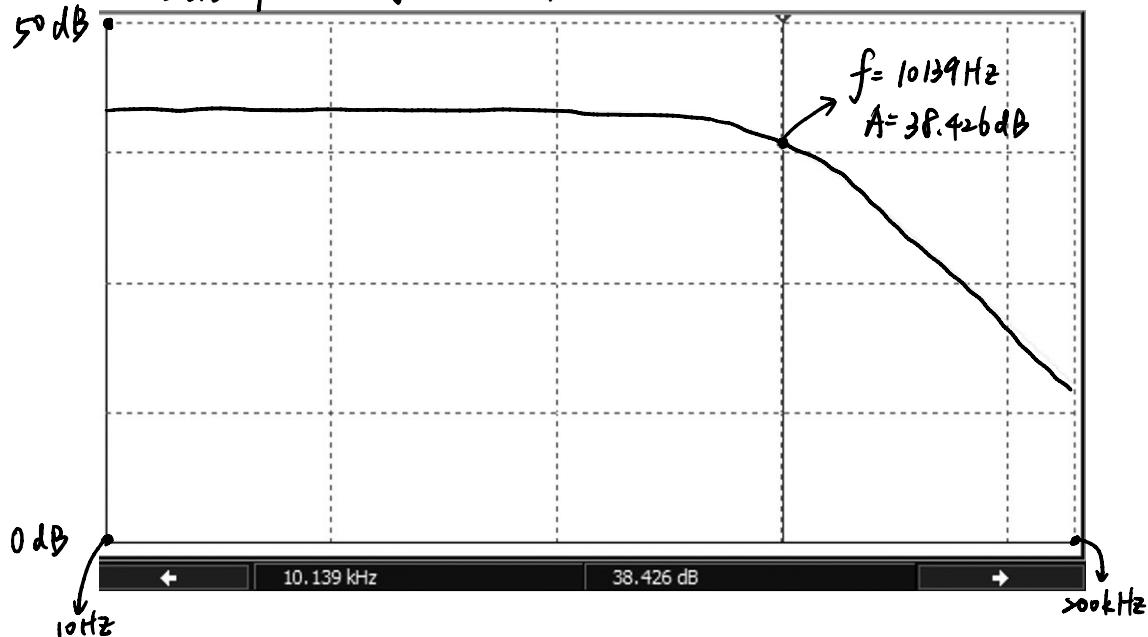-3 dB point at $f \approx 10000\text{ Hz}$, $A = 38.426\text{ dB} \approx 83.42\%$




Bode Plot - Phase Response

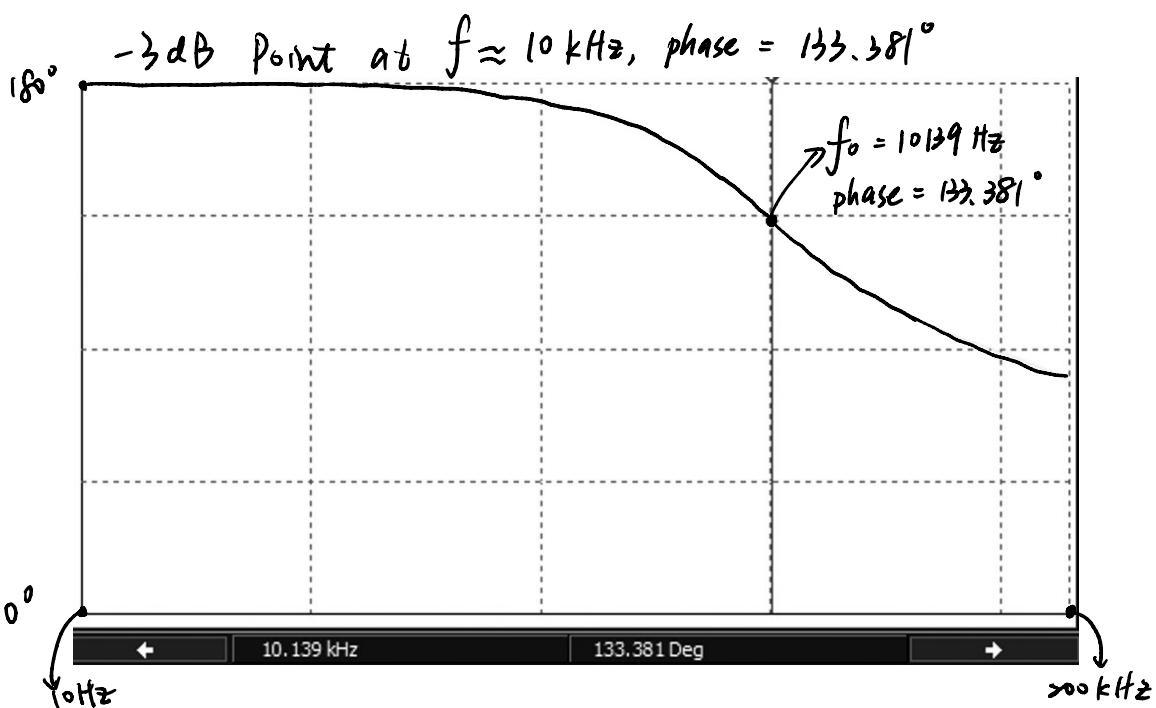Phase at peak gain (10Hz) is 180° (out of phase)




2. Common mode circuit diagram

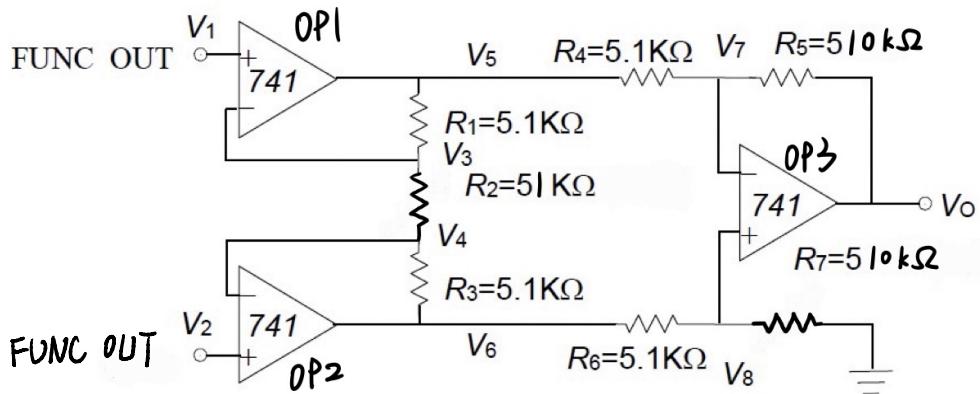

Input 100Hz, 1Vp.p. $A_{100Hz} \approx 0.99\%$


LabVIEW

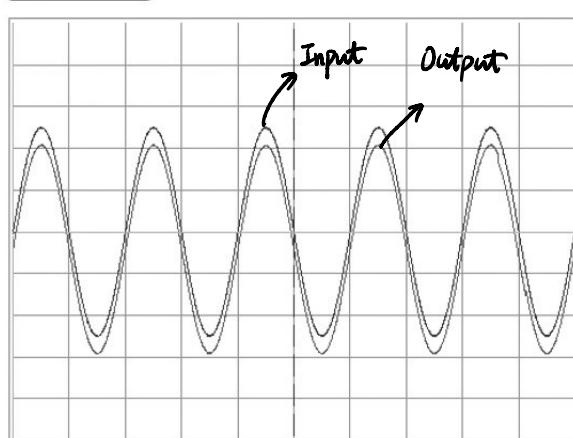

CH0 Meas: RMS: 353.04 mV Freq: 100.020 Hz Vp-p: 1.005 V
CH1 Meas: RMS: 362.38 mV Freq: 100.080 Hz Vp-p: 1.003 V


Input 10kHz, 1Vpp $A_{10kHz} \approx 0.81\%$

LabVIEW

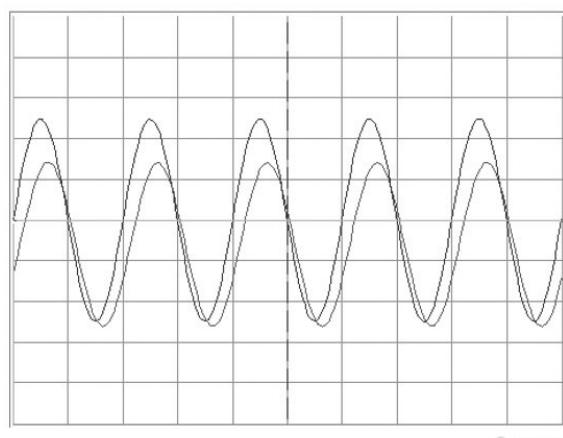

CH0 Meas: RMS: 350.98 mV Freq: 10.000 kHz Vp-p: 996.67 mV
CH1 Meas: RMS: 308.77 mV Freq: 10.003 kHz Vp-p: 808.80 mV

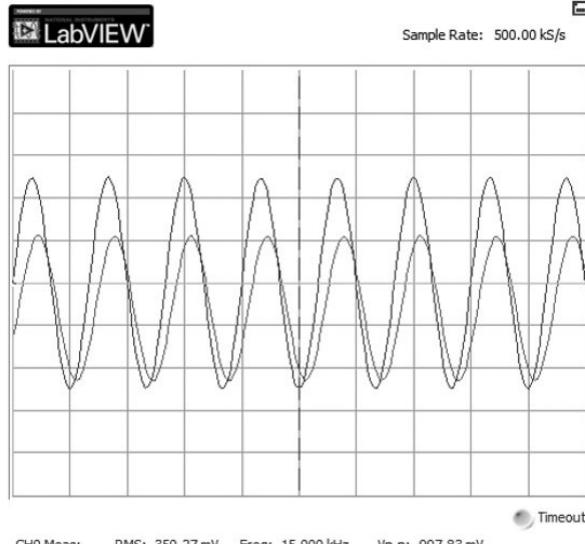Input = 15 kHz, 1Vp.p. $A_{15\text{kHz}} = 0.68\%$





Common mode gain

| Input f | Gain |
|---------|------------------------------------|
| 100Hz | 0.99 % $\approx -0.087 \text{ dB}$ |
| 10kHz | 0.81 % $\approx -1.83 \text{ dB}$ |
| 15kHz | 0.68 % $\approx -2.34 \text{ dB}$ |


Bode Plot on common mode

Peak gain at 10 Hz $A \approx -0.01 \text{ dB}$

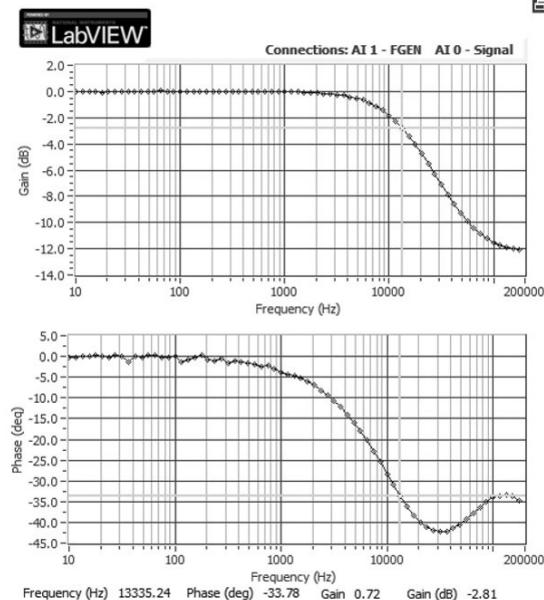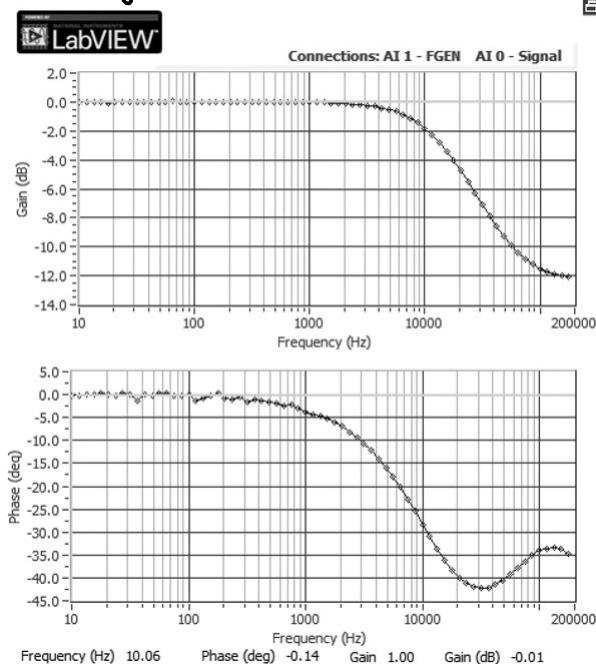-3dB point at $f_0 \approx 13 \text{ kHz} A \approx -2.81 \text{ dB}$







Bode Plot on higher frequency.

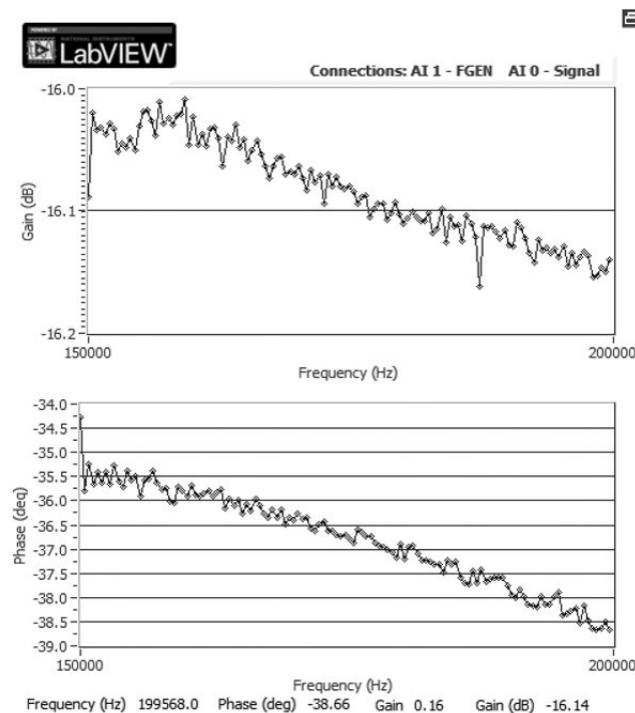

Common mode multism simulation:

Schematic:

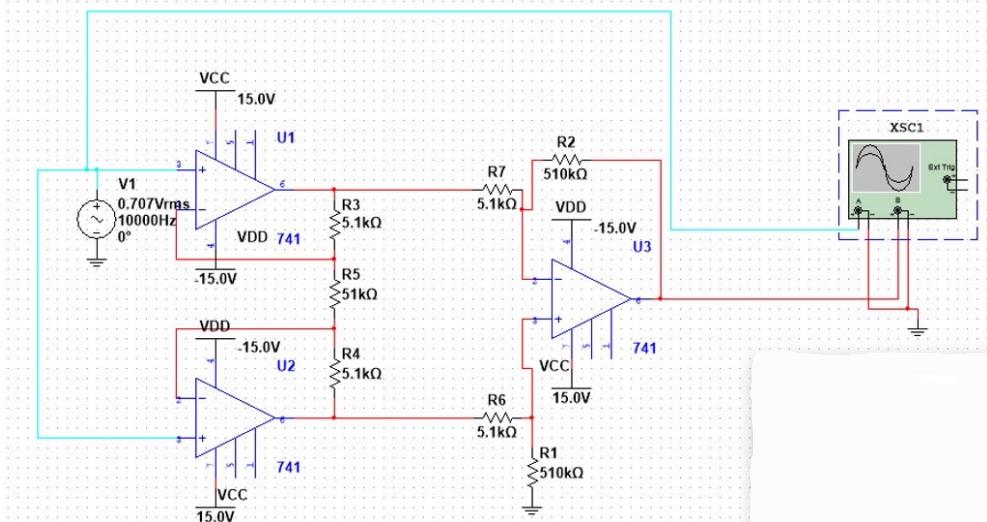

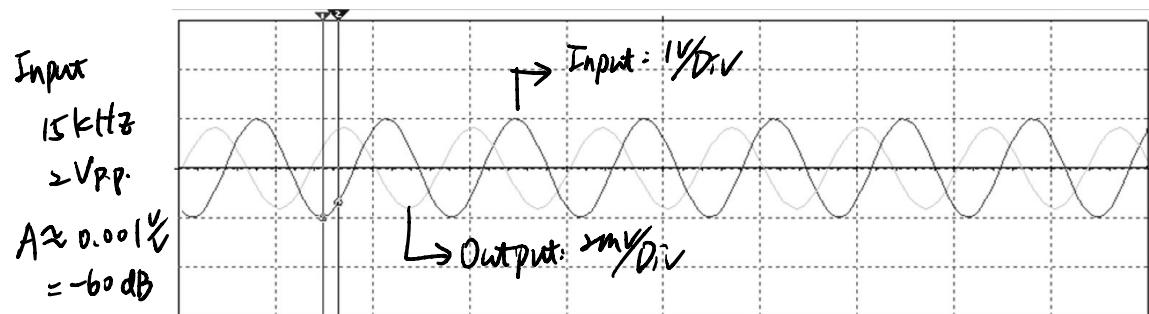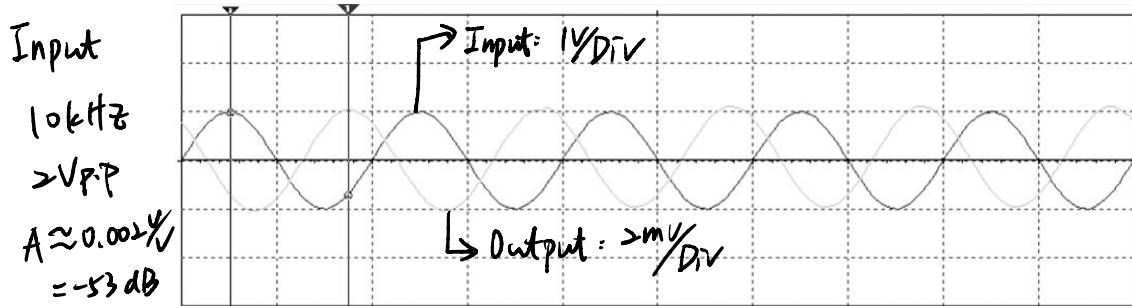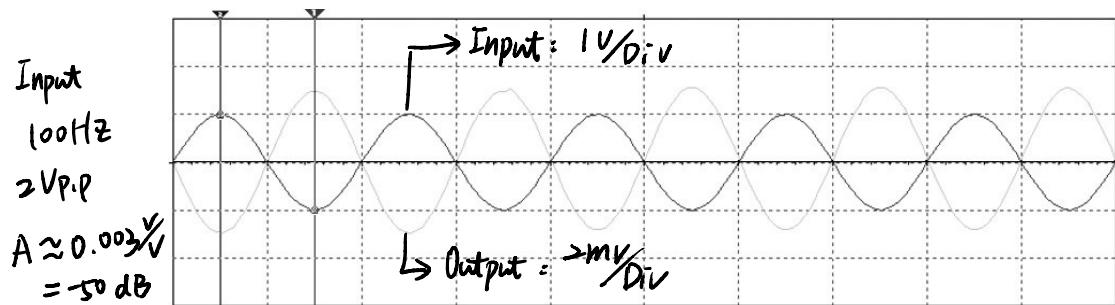


At 3 different frequencies, gains are all less than -50 dB .

Bode Plot - Magnitude Response

Peak gain at 10 Hz, $A = -50.529 \text{ dB}$


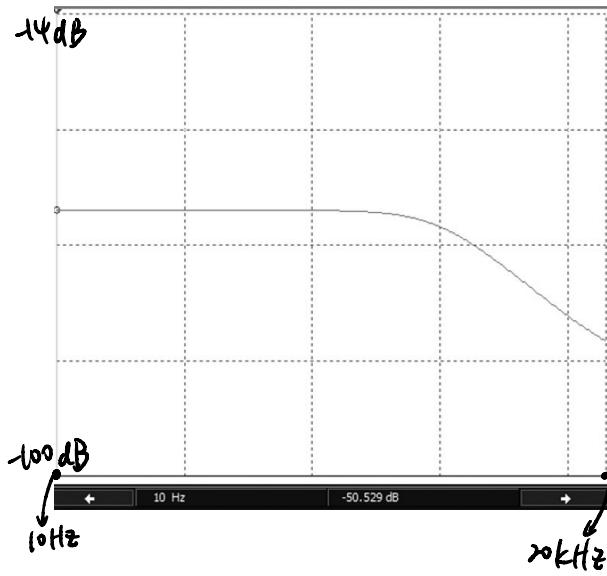
$\rightarrow -3 \text{ dB}$ point at $f_0 = 9.643 \text{ kHz}$, $A = -53.449 \text{ dB}$



Bode Plot - Phase Response

Phase = 179.939° at peak gain

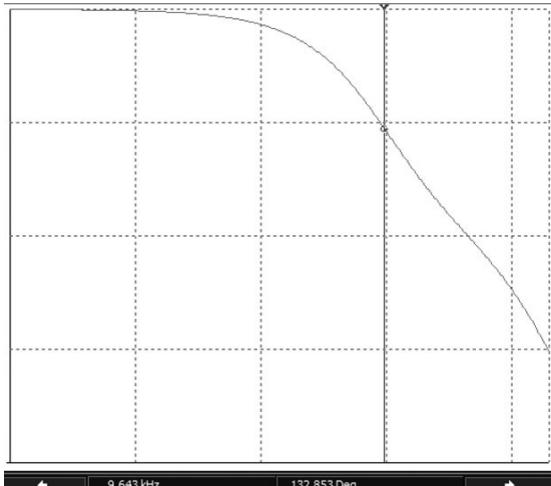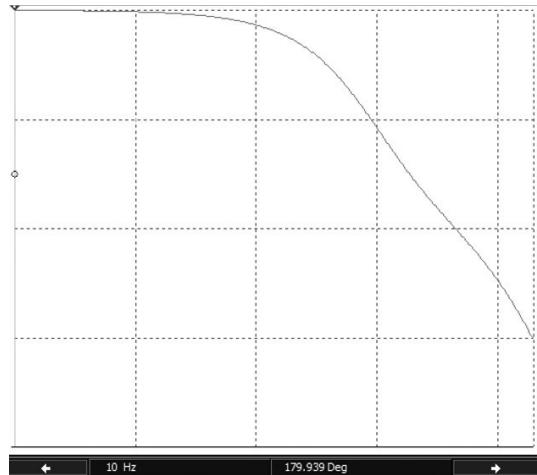$\rightarrow -3 \text{ dB}$ point, phase = 132.853°



* Result

Differential Mode:

<a> Physical circuit

| f | Gain (V/V) | Bode Plot Gain |
|-------|------------|-------------------|
| 100Hz | 110 | 41 dB ≈ 112 (V/V) |
| 10kHz | 85 | 38 dB ≈ 80 (V/V) |
| 15kHz | 72 | 36 dB ≈ 63 (V/V) |

* Simulation*

| f | Gain (V/V) | Bode Plot Gain |
|-------|------------|-------------------------|
| 100Hz | 120 | 41.6 dB ≈ 120 (V/V) |
| 10kHz | 80 | 38.426 dB ≈ 83.42 (V/V) |
| 15kHz | 60 | 35.98 dB ≈ 63 (V/V) |

Result of physical and simulation on differential mode are matched.

Common Mode:

<a> Physical circuit


| f | Gain (V/V) | Bode Plot Gain |
|-------|------------|-----------------------|
| 100Hz | 0.99 | -0.01 dB ≈ 0.99 (V/V) |
| 10kHz | 0.81 | -2 dB ≈ 0.79 (V/V) |
| 15kHz | 0.68 | -3.5 dB ≈ 0.66 (V/V) |

* Simulation*

| f | Gain (V/V) | Bode Plot Gain |
|-------|------------|---------------------------|
| 100Hz | 0.003 | -50.529 dB ≈ 0.0029 (V/V) |
| 10kHz | 0.002 | -53.449 dB ≈ 0.0021 (V/V) |
| 15kHz | 0.001 | -60 dB ≈ 0.001 (V/V) |

Result of physical circuit didn't match the simulation.

Error in common mode :

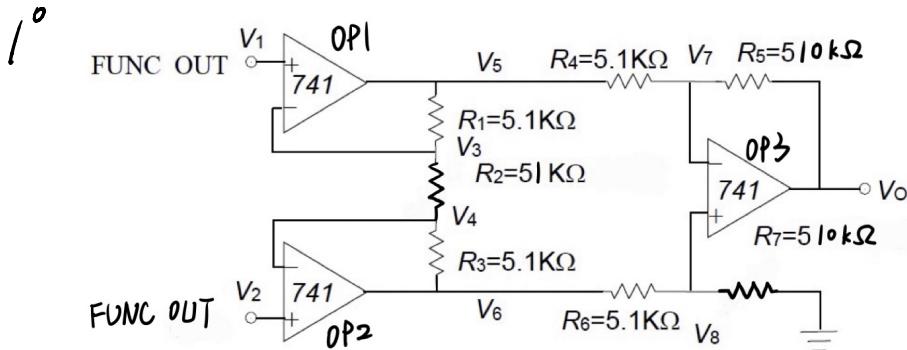

Connecting the signal from the function generator to physical circuit using the different lengths of solid wires might cause a propagation delay, which causes a phase shift between two inputs to OP1 and OP2. When subtracting the signal on the last stage differential amplifier, have no the same signal to subtract so the result will be amplified by R_5/R_4 , and therefore the output signal will not be ideal.

2° Using large value of resistors on R_5 and R_7 might not be a good choice. Since there exists error on resistor value, it might not satisfied the condition $\frac{R_5}{R_4} = \frac{R_7}{R_6}$, so that the last stage will no longer become the differential amplifier.

3° It is confident that we didn't connect the circuit in the wrong way, since the result of the differential mode is correct. The small change between differential mode and common mode is connect V_2 to function generator.

Question and Discussion:

1. Refer to the datasheet of uA741 Op Amp; please list the parameters of the following, input resistance (輸入電阻), input capacitance (輸入電容), unit-gain bandwidth, and DC gain (直流增益).

Input resistance: ($T_A = 25^\circ C, V_S = \pm 20V$) $\left\{ \begin{array}{l} \text{MIN: } 0.3 M\Omega \\ \text{TYP: } 2 M\Omega \end{array} \right.$

Input capacitance: ($T_A = 25^\circ C$) 1.4 pF

Unit-gain bandwidth: ($T_A = 25^\circ C$) $\left\{ \begin{array}{l} \text{MIN: } 0.437 \text{ MHz} \\ \text{TYP: } 1.5 \text{ MHz} \end{array} \right.$

DC gain: 106 dB

2. Refer to Figure 1 circuit diagram; if $R_1/R_4 \neq R_2/R_3$, then V_o equals to what?

Using superposition rule:

1° turn off V_2 ($V_+ = V_- = 0$)

$$\Rightarrow \frac{V_1 - V_-}{R_1} = \frac{V_- - V_{out-}}{R_4}$$


$$\Rightarrow V_{out-} = - \frac{R_4}{R_1} V_1$$

2° turn off V_1 ($V_+ = V_- = V_2 \cdot \frac{R_3}{R_2 + R_3}$)


$$\Rightarrow V_{out+} = V_2 \frac{R_3}{R_2 + R_3} \left(1 + \frac{R_4}{R_1} \right)$$

3° $V_{out} = V_{out-} + V_{out+}$
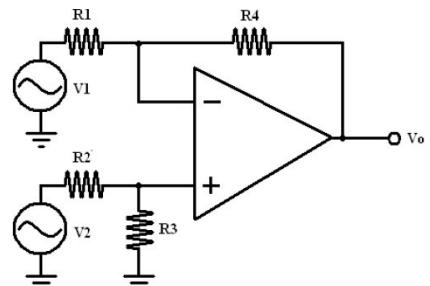
$$= - \frac{R_4}{R_1} V_1 + V_2 \frac{R_3}{R_2 + R_3} \left(1 + \frac{R_4}{R_1} \right)$$



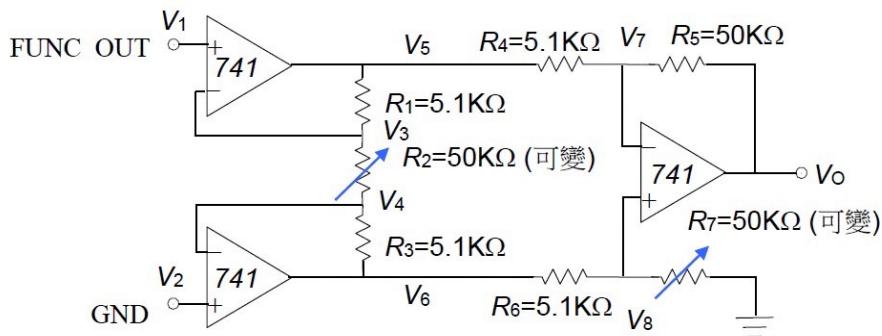3. Refer to Figure 2 circuit diagram; if the R_2 and R_7 design of the differential amplifier is adjustable, what do R_2 and R_7 mean?



$$Av = \frac{V_o}{V_2 - V_1} = \left(1 + \frac{2R1}{R2} \right) \cdot \frac{R5}{R4} \quad (\text{if } \frac{R5}{R4} = \frac{R7}{R6})$$

R_2 is a gain factor in the first stage.

If R_7 no longer match R_5 : match or mismatch R_5 to perform different behavior.

4. When building a circuit on the breadboard versus on the printed circuit board (印刷電路板), which circuit board can function at a higher frequency? Why?

Printed circuit board (PCB) can function at a high frequency.

Because high-frequency PCB transmit electromagnetic waves need less energy than breadboard. Also, with low dielectric constant, PCB ensure smooth frequency transmission and minimum signal delay.